

1.)

$$\text{a.) } (D + 2.5) y(t) = 0$$

$$\lambda = -2.5$$

$$\underline{y(t)} = \underline{3e^{-2.5t}}$$

$$C_1 e^{-2.5t}$$

$$C_1 e^0 = 3$$

$$C_1 = 3$$

$$2) (D^3 + 0.6D^2 + 25.1125D + 25063) y(t) = 0$$

$$y_0(0) = 1.5, \quad y_0'(0) = 2, \quad y_0''(0) = -1$$

use Matlab to solve for Roots

$$\lambda = -0.1$$

$$-0.1, -0.25 + j\sqrt{5}, -0.25 - j\sqrt{5}$$


$$\lambda = -0.25 + j\sqrt{5}$$

$$\lambda = -0.25 - j\sqrt{5}$$

$$C_1 e^{-0.1t} + C_2 e^{(-0.25+j\sqrt{5})t} + C_3 e^{(-0.25-j\sqrt{5})t}$$

using matlab to solve and find
equation 1.
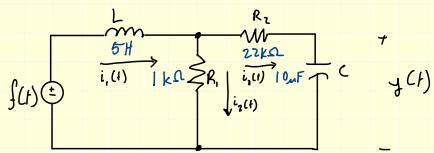
$$x_{\Delta t} = \left(\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} + \Delta t \cdot \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -25063 & -25.1125 & -0.6 \end{bmatrix} \right) \begin{bmatrix} 1.5 \\ 2 \\ -1 \end{bmatrix}$$



(a)

$$i_1(t) = i_2(t) + i_3(t)$$

$$i_2(t) = \frac{V - y(t)}{R_2} = C \frac{dy(t)}{dt} + y(t)$$

$$i_3(t) = \frac{V}{R_1}$$

$$i_1 = \frac{V}{R_1} + \frac{V - y(t)}{R_2}$$

$$\frac{di_1(t)}{dt} = \frac{1}{R_1} \frac{dv}{dt} + \frac{1}{R_2} \left(\frac{dv}{dt} - \frac{dy(t)}{dt} \right)$$

$$f(t) = L \frac{di_1(t)}{dt} + v$$

$$f(t) = L \left[\frac{1}{R_1} \frac{dv}{dt} + \frac{1}{R_2} \left(\frac{dv}{dt} - \frac{dy(t)}{dt} \right) \right] + V$$

$$f(t) = L \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \frac{dv}{dt} - \frac{L}{R_2} \frac{dy(t)}{dt} + V$$

$$V = y + CR_2 \frac{dy}{dt} \Rightarrow \frac{dv}{dt} = \frac{dt}{dt} + CR_2 \frac{d^2 y}{dt^2}$$

$$f(t) = L \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \left(\frac{dy}{dt} + CR_2 \frac{d^2 y}{dt^2} \right) - \frac{L}{R_2} \cdot \frac{dy}{dt} + y + CR_2 \frac{dy}{dt}$$

use D operators

$$f(t) = D L \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + D^2 L C R_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - D \frac{L}{R_2} + y + D C R_2$$

$$f(t) = \underline{D^2 L C R_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + D \left(\frac{L}{R_1} + C R_2 \right) + y}$$

(b)

$$L = 5H$$

$$1.1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) D^2 + (0.005 + 0.22) D + y$$

$$C = 10\mu F$$

$$\frac{23}{20000} D^2 + \frac{9}{40} D + y$$

$$R_2 = 22k\Omega$$

$$v = CR_2 \left(\frac{dy}{dt} \right) + y(t)$$

$$R_1 = 1k\Omega$$

$$\lambda_1 = -4.5503$$

$$i_1(0) = \frac{y(0)}{R_1} + \left(\frac{R_2 C}{R_1} \right) y'(0)$$

$$y(0) = 5V$$

$$i_1 e^{-4.5503t} + C_2 e^{-191.1019t} = 0$$

$$i_1(0) = 0.2A$$

$$\underline{\underline{= 847.83}}$$

$$i_1(0) = 0.2 - \frac{5}{1000}$$

(c)

$$C_1 + C_2 = 5$$

$$-4.5503 C_1 + -191.1019 C_2 = 847.83$$

$$\begin{bmatrix} 1 & 1 & 5 \\ -4.5503 & -191.1019 & 847.83 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 0 & -181.105 \\ 0 & 1 & -4.5503 \end{bmatrix}$$

$$\underline{\underline{9.6667 e^{-4.5503t} - 4.667 e^{-191.1019t}}}$$

(d)

$$\left(\begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} + \Delta t \cdot \begin{bmatrix} 0 & 1 \\ -869.57 & -195.651 \end{bmatrix} \right) \cdot \begin{bmatrix} 5 \\ 847.83 \end{bmatrix}$$