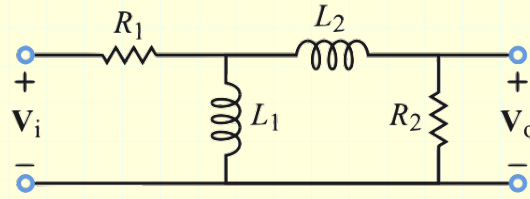


**Problem 3.30 :**

**Given:** The values  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$ ,  $L_1 = 1mH$ , and  $L_2 = 2mH$ ; and given the circuit below




**Find:**

- $H(s) = \frac{V_o}{V_i}$
- $h(t)$

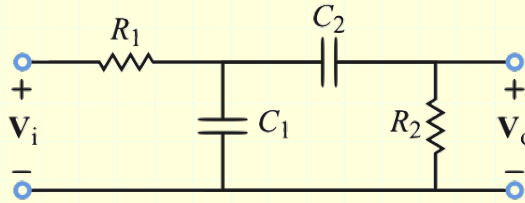**Problem 3.31 :**

**Given:** The values  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$ ,  $C_1 = 1\mu F$ , and  $C_2 = 2\mu F$ ; and given the circuit below




**Find:**

- $H(s) = \frac{V_o}{V_i}$
- $h(t)$

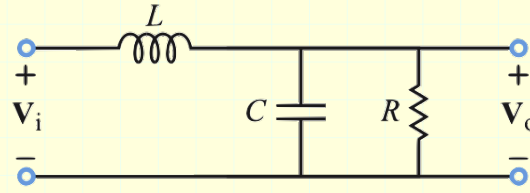**Problem 3.32 :**

**Given:** The values  $R = 5\Omega$ ,  $L = 0.1mH$  , and  $C = 1\mu F$ ; and given the circuit below



a.  $H(s) = \frac{V_o}{V_i}$

b.  $h(t)$

**Find:**

**Problem 3.33 :**

**Given:** An LTI system is described by the LCCDE

$$\frac{d^2y}{dt^2} - 5\frac{dy}{dt} + 6y = \frac{dx}{dt} + 5x. \quad (1)$$

**Find:** Is the system BIBO stable?


**Problem 3.36 :****Given:** An LTI system has transfer function

$$H(s) = \frac{(s+1)(s+2)}{s(s+3)} \quad (2)$$

**Find:** Is it BIBO stable?

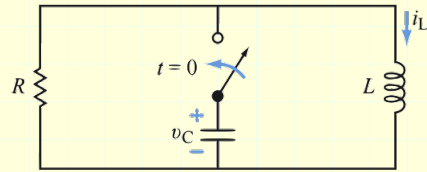**Problem 4.8 :**


**Given:** Before closing the switch  $v_C(0^-) = 24V$ . Also, the element values are  $R = 1\Omega$ ,  $L = 0.8H$ , and  $C = 0.25F$ .



**Find:** The equation for  $i_L(t)$

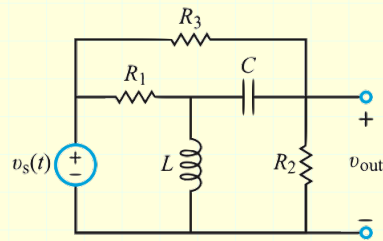**Problem 4.9 :**


**Given:** The values  $V_s(t) = 11u(t)$  V.  $R_1 = 2\ \Omega$ ,  $R_2 = 4\ \Omega$ ,  $R_3 = 6\ \Omega$ ,  $L = 1$  H, and  $C = 0.5$  F with the circuit below.



**Find:** The voltage  $v_{out}$ .

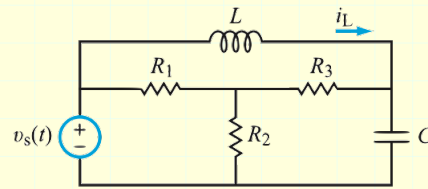**Problem 4.11 :**

**Given:** The values  $v_s(t) = 44u(t)$  V,  $R_1 = 2\ \Omega$ ,  $R_2 = 4\ \Omega$ ,  $R_3 = 6\ \Omega$ ,  $C = 0.1$  F, and  $L = 4$  H with the circuit below.




**Find:** Using mesh-current analysis in the s-domain find  $i_L(t)$  in the circuit above.



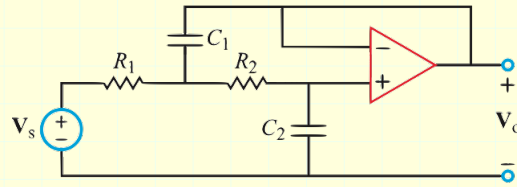**Problem 4.32 :**

**Given:** The values  $R_1 = R_2 = 100\ \Omega$  and  $C_1 = C_2 = 1\ \mu F$  with the circuit below.




**Find:**

- $H(s) = \frac{V_o}{V_s}$
- $h(t)$

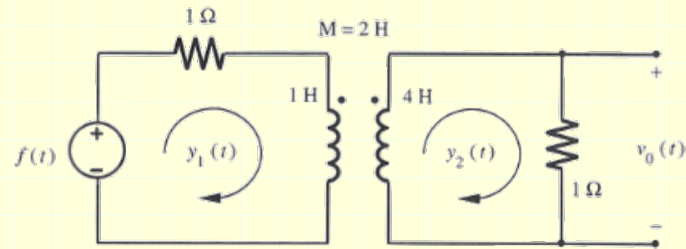**Problem 11. :**

**Given:** The system is in zero state initially. Assume that the primary and secondary sides of the transformer are electrically connected to the same ground. The input voltage is  $f(t) = 100u(t)$ .



**Find:**  $v_0(t)$  for  $t \geq 0$  in the above circuit.