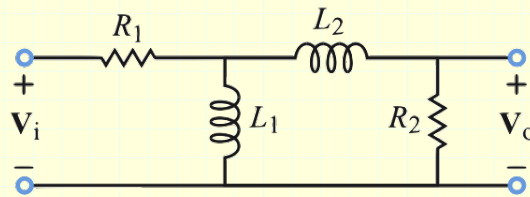


**Problem 3.30 :**

**Given:** The values  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$ ,  $L_1 = 1mH$ , and  $L_2 = 2mH$ ; and given the circuit below




**Find:**

- $H(s) = \frac{V_o}{V_i}$
- $h(t)$

Answer Section

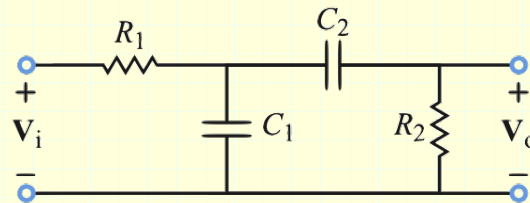**Problem 3.31 :**

**Given:** The values  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$ ,  $C_1 = 1\mu F$ , and  $C_2 = 2\mu F$ ; and given the circuit below




**Find:**

- $H(s) = \frac{V_o}{V_i}$
- $h(t)$

Answer Section

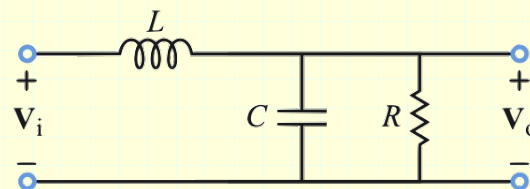**Problem 3.32 :**

**Given:** The values  $R = 5\Omega$ ,  $L = 0.1mH$ , and  $C = 1\mu F$ ; and given the circuit below



- $H(s) = \frac{V_o}{V_i}$
- $h(t)$

	October 11, 2025	3620, Assignment: 7	Petersen, Kelson	2/ 3
	<p><b>Find:</b></p>			
	Answer Section			
	<p><b>Problem 3.33 :</b></p>			
	<p><b>Given:</b></p>			
	<p><b>Find:</b></p>			
	Answer Section			
	<p><b>Problem 3.36 :</b></p>			
	<p><b>Given:</b></p>			
	<p><b>Find:</b></p>			
	Answer Section			
	<p><b>Problem 4.8 :</b></p>			
	<p><b>Given:</b></p>			
	<p><b>Find:</b></p>			
	Answer Section			
	<p><b>Problem 4.9 :</b></p>			
	<p><b>Given:</b></p>			
	<p><b>Find:</b></p>			
	Answer Section			
	<p><b>Problem 4.11 :</b></p>			
	<p><b>Given:</b></p>			
	<p><b>Find:</b></p>			
	Answer Section			
	<p><b>Problem 4.32 :</b></p>			
	<p><b>Given:</b></p>			
	<p><b>Find:</b></p>			
	Answer Section			
	<p><b>Problem 11. :</b></p>			
	<p><b>Given:</b></p>			
	<p><b>Find:</b></p>			

## Answer Section